



tiec



efabless.com

University of
Hertfordshire **UH**



جامعة الملك فهد للبترول والمعادن
King Fahd University of Petroleum & Minerals

Schematic Design and Simulation (IC Design Flow)

Dr. Ahmed Reda Mohamed^{1,2}

¹IRC for Communication Systems and Sensing, King Fahd University of Petroleum & Minerals, Dhahran 31261, Saudi Arabia

²PhD, The MoE Key Laboratory of Artificial Intelligence & Bio-Circuits and Systems Laboratory (*BiCASL*), Department of Micro-Nano Electronics, Shanghai Jiao Tong University, Shanghai, China.

Outlines



- ☐ Objective
- ☐ CMOS Inverter
- ☐ Schematic Editor
- ☐ Create Symbol
- ☐ Testbench
- ☐ Cadence Hot Keys
- ☐ Discussion

Outlines




- ☐ **Objective**
- ☐ **CMOS Inverter**
- ☐ **Schematic Editor**
- ☐ **Create Symbol**
- ☐ **Testbench**
- ☐ **Cadence Hot Keys**
- ☐ **Discussion**

Objective (1/2)


Objective

- Create a schematic and symbol for a CMOS inverter in **Cadence Virtuoso**.
- Perform **simulations** for the inverter


Discrete Element

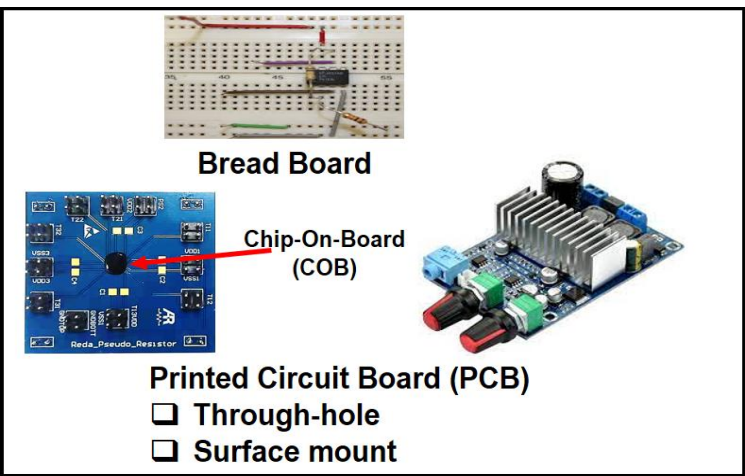


Vey large Scale Integrated Circuit

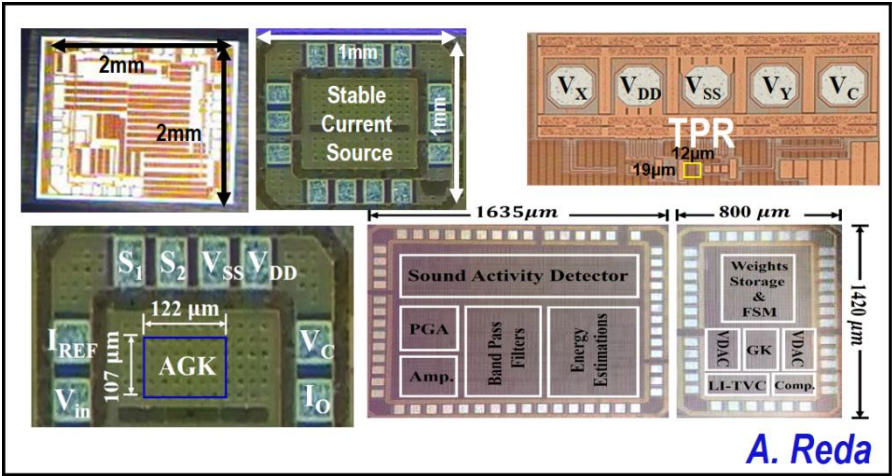



Item	Discrete Element	Very large scale Integrated Circuit
Area	Large	Small
Configuration	Easy	Complex
Price	Cheap	Expensive
Applications	Small production	Mass production
Power consumption	High	Low

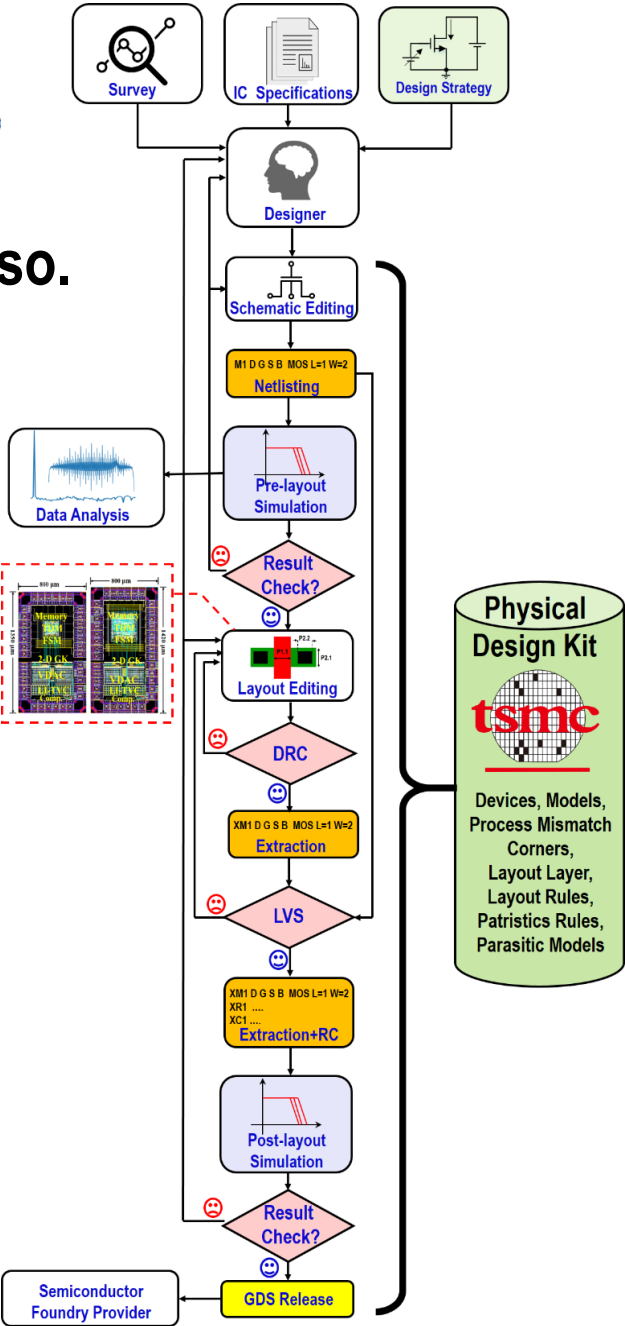


Objective (2/2)

 

 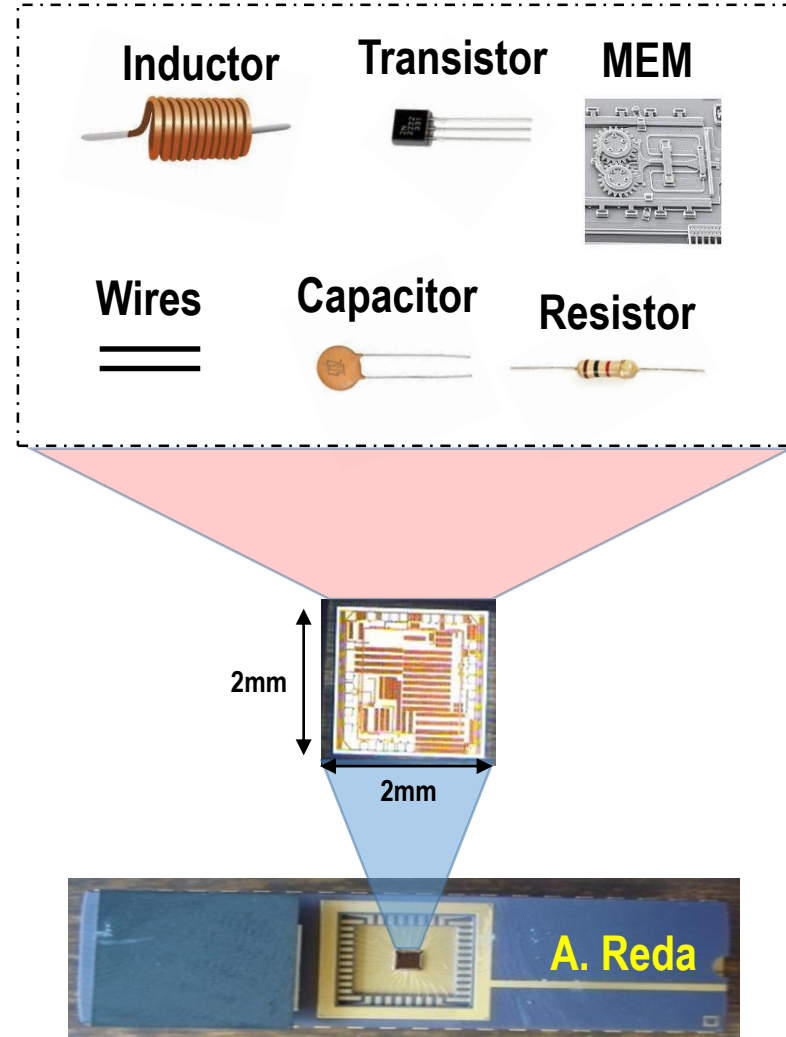❑ An **integrated circuit (IC)** is a set of electronic circuits on one small flat piece (or "chip") of semiconductor material, usually silicon.



Layout using CAD tool

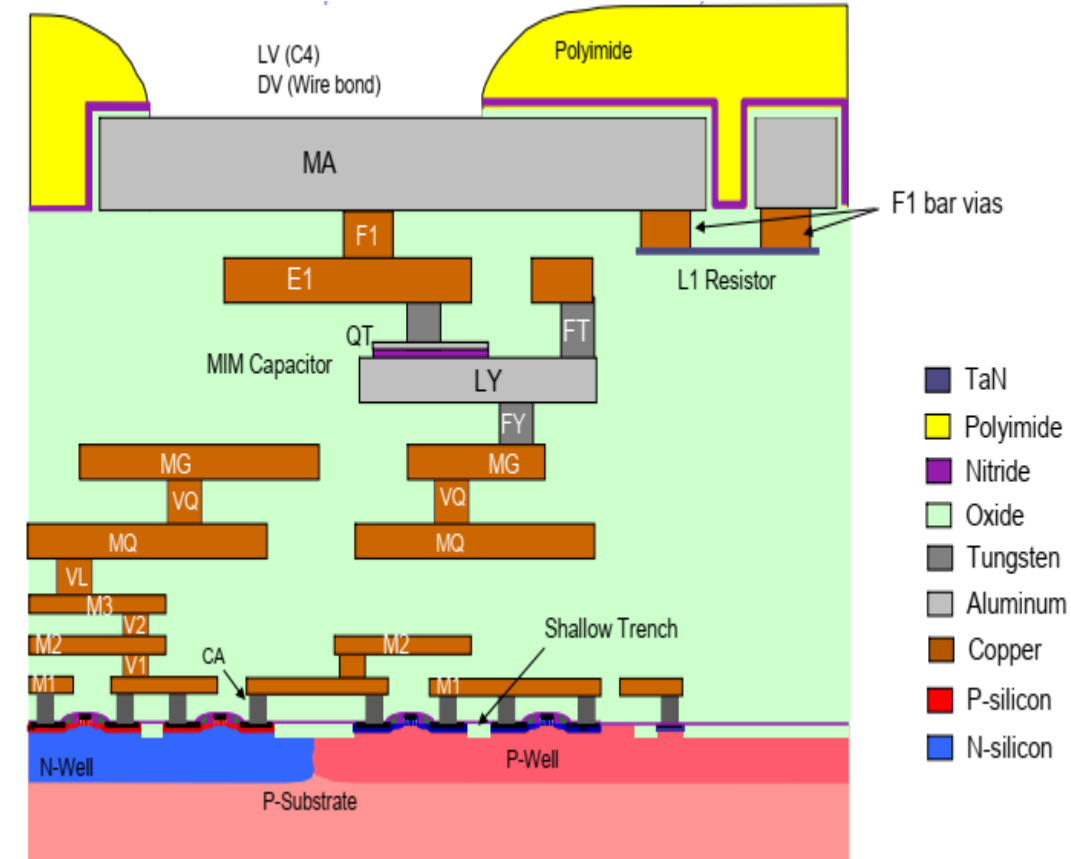





Process Cross-Section
8 layers

Outlines



- ☐ Objective
- ☒ **CMOS Inverter**
- ☐ Schematic Editor
- ☐ Create Symbol
- ☐ Testbench
- ☐ Cadence Hot Keys
- ☐ Discussion

CMOS Inverter (1/2)

    

$$B_n = \mu_n C_{ox} \frac{W_n}{L_n}$$

B_n : Gain process factor of n-MOSFET
 μ_n : Mobility of Electron
 C_{ox} : Gate Oxide Capacitor/unit area
 W_n : width of transistor
 L_n : length of transistor





$$B_p = \mu_p C_{ox} \frac{W_p}{L_p}$$

B_p : Gain process factor of p-MOSFET
 μ_p : Mobility of Hole
 C_{ox} : Gate Oxide Capacitor/unit area
 W_p : width of transistor of p-MOSFET
 L_p : length of transistor of p-MOSFET

$$V_{thg} = \frac{V_{th,n} + r(V_{DD} + V_{th,p})}{1 + r}$$

$$\text{Where } r = \sqrt{\frac{\beta_p}{\beta_n}}$$

CMOS Inverter (2/2)

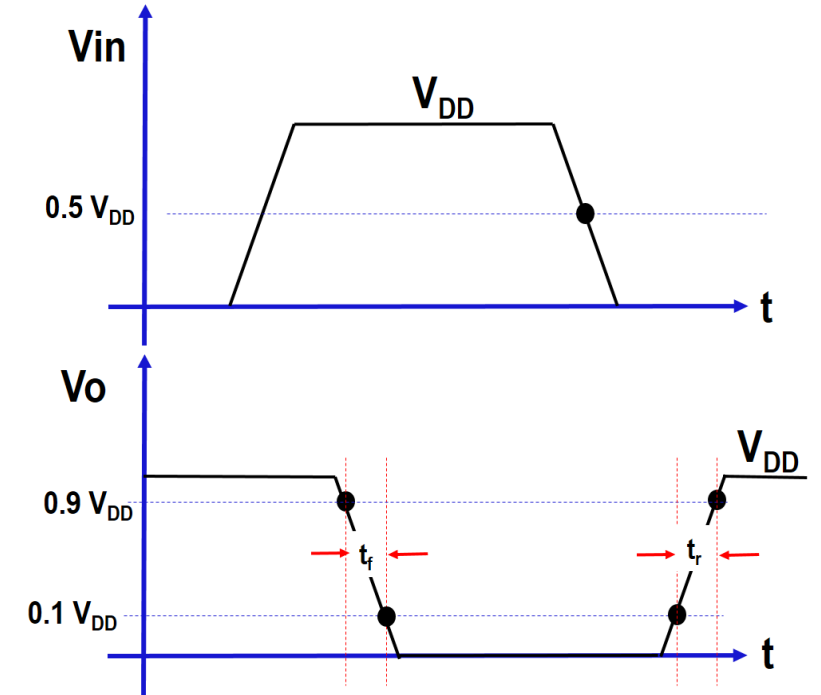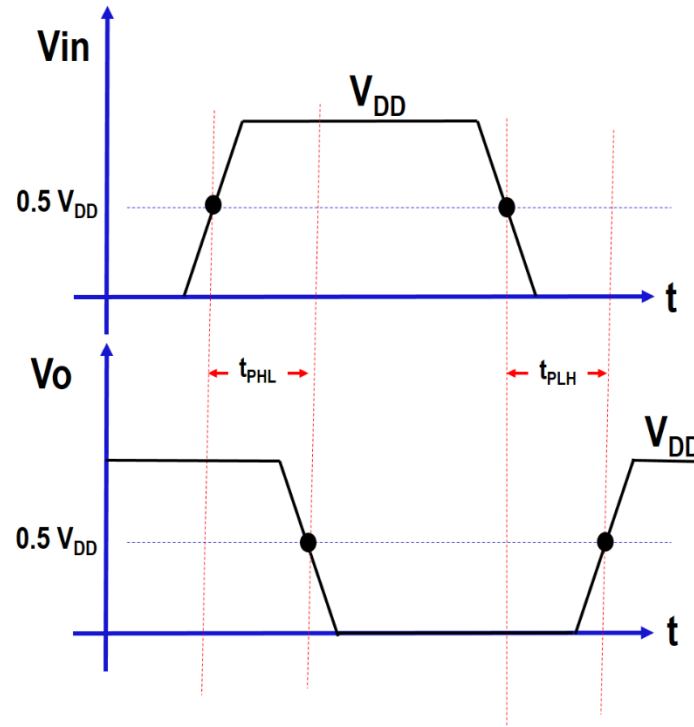  

- ❑ **Propagation time (t_p):** is the time between 50 % of the input voltage to 50 % of the output.

$$t_p = \frac{(t_{PHL} + t_{PLH})}{2}$$

- ❑ t_{PHL} : is the propagation time from high to low.
- ❑ t_{PLH} : is the propagation time from low to high.

- ❑ **Rise time (t_r):** is the time between 10% of the output voltage to 90 % of the output.

- ❑ **Fall time (t_f):** is the time between 90% of the output voltage to 10% of the output

Outlines



- ☐ Objective
- ☐ CMOS Inverter
- ☐ **Schematic Editor**
- ☐ Create Symbol
- ☐ Testbench
- ☐ Cadence Hot Keys
- ☐ Discussion


Schematic Editor (1/4)




- ❑ Open a terminal and write “virtuoso &”

```
cadence@berkeley: ~/my_project/tsmc_180
File Edit View Search Terminal Help
cadence@berkeley:~/my_project/tsmc_180$ virtuoso &
[1] 1503
```


- ❑ Select “File”

 


- ❑ From new → library

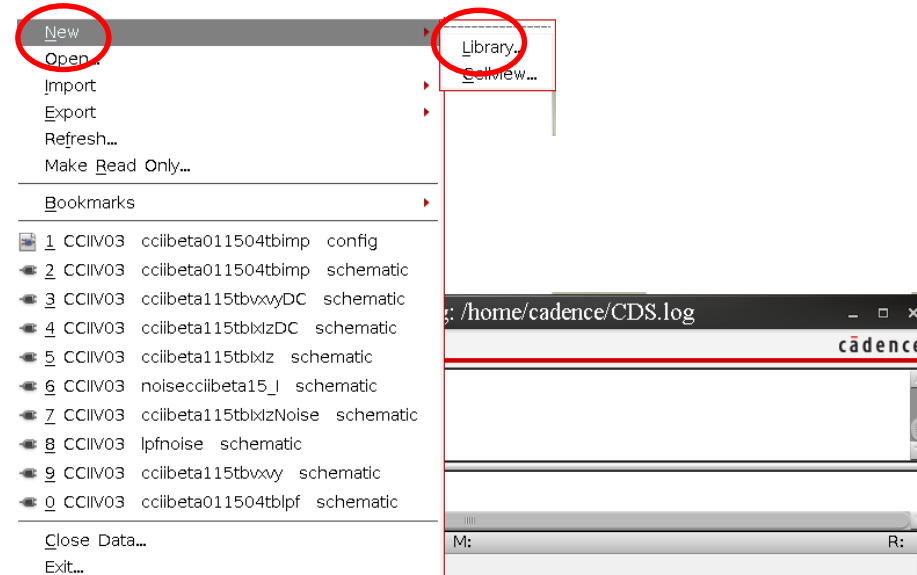

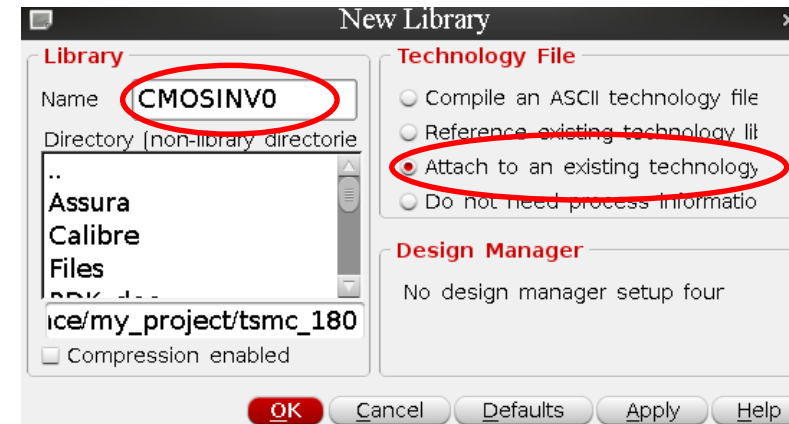- ❑ Write library's name and select “attach to an existing technology”



 
- ❑ Then, select technology library “tsmc18rf”, and press “OK”




Schematic Editor (2/4)





❑ From File → new → Cellview

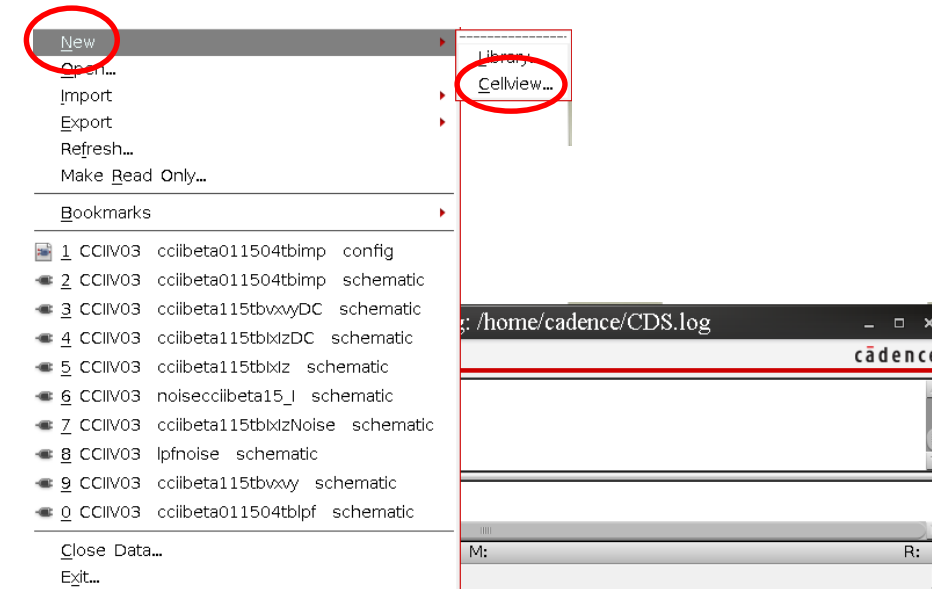

❑ Write name of the cell

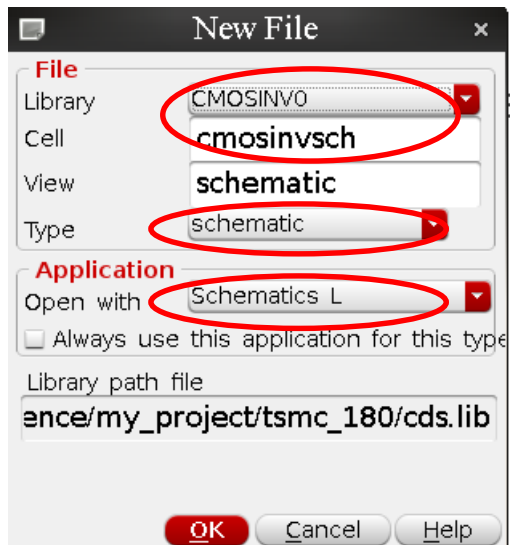

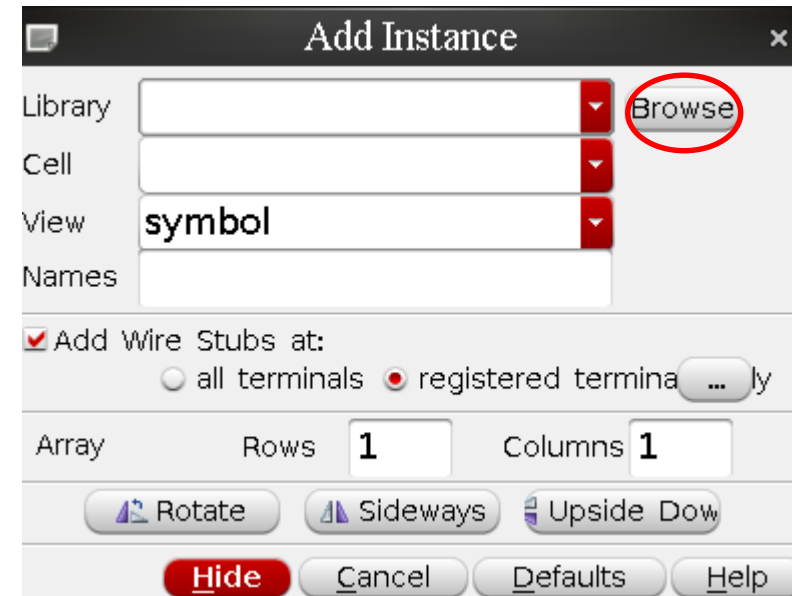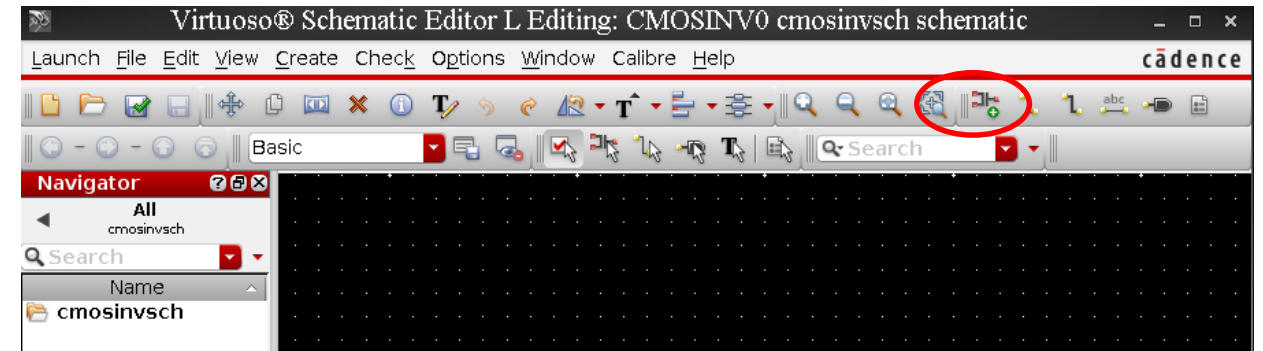
❑ Then, start to add the instances (MOSFET)




Schematic Editor (3/4)



❑ Select tsmc18rf→nmos2v→symbol

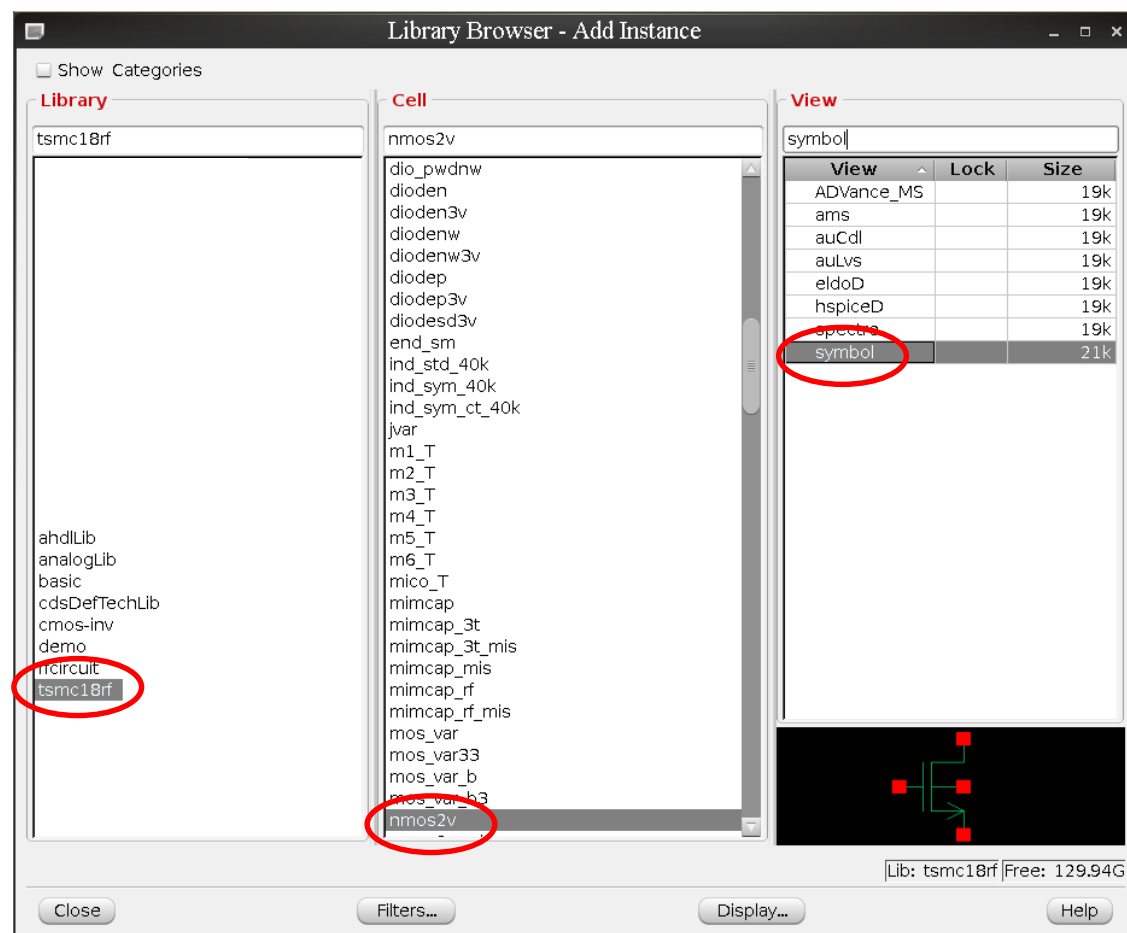




❑ Select tsmc18rf→pmos2v→symbol

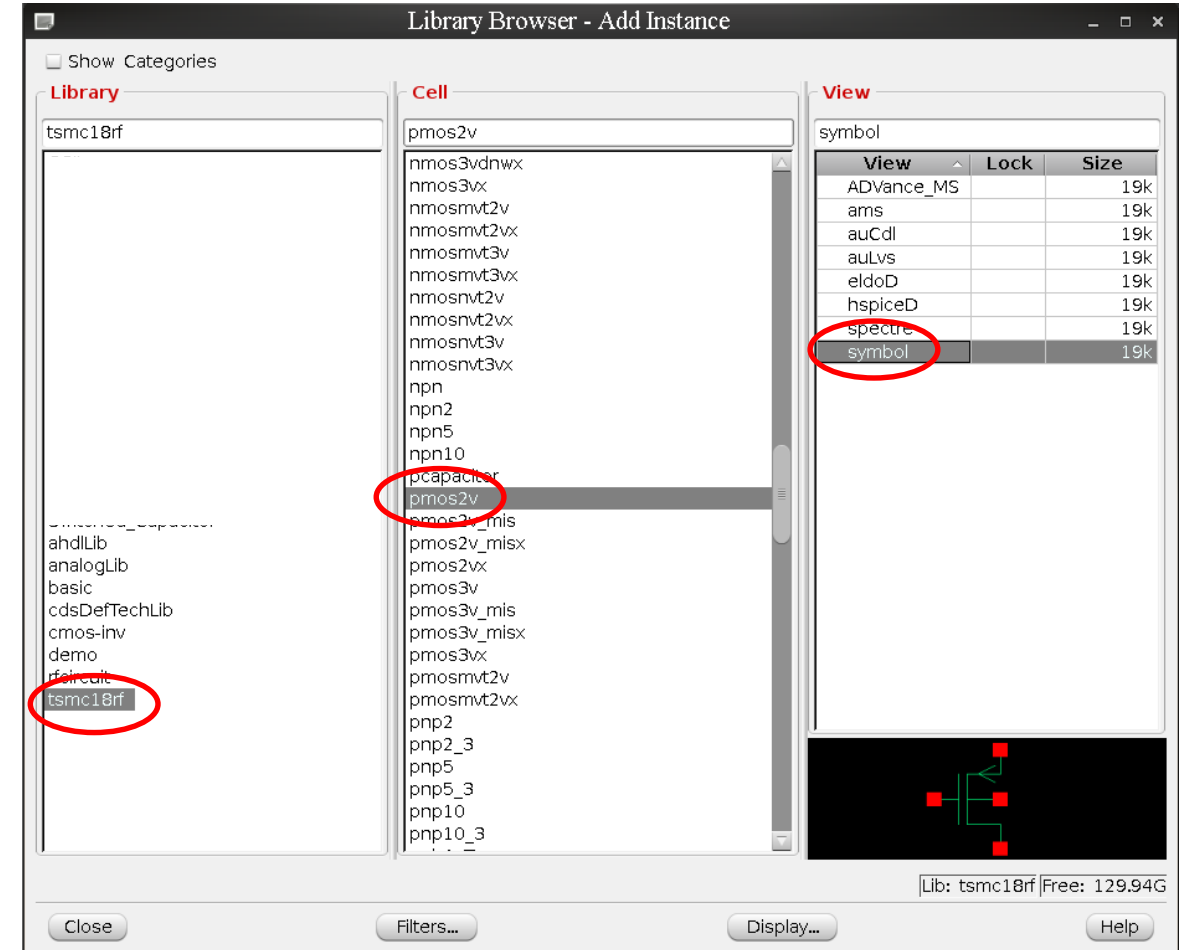





Schematic Editor (4/4)

  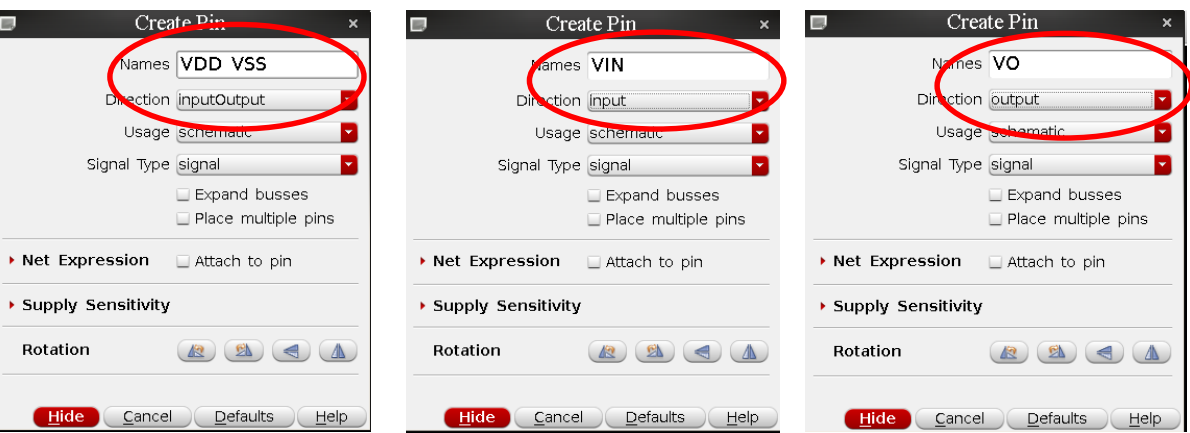- Start to wire the instances using key “w” and add pins by using “p”




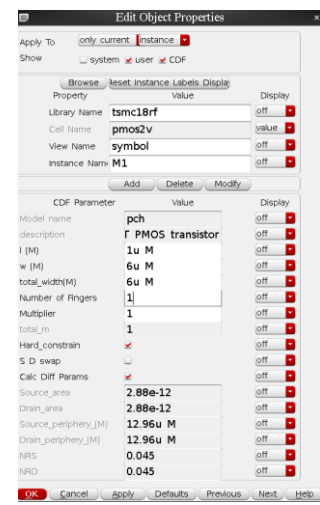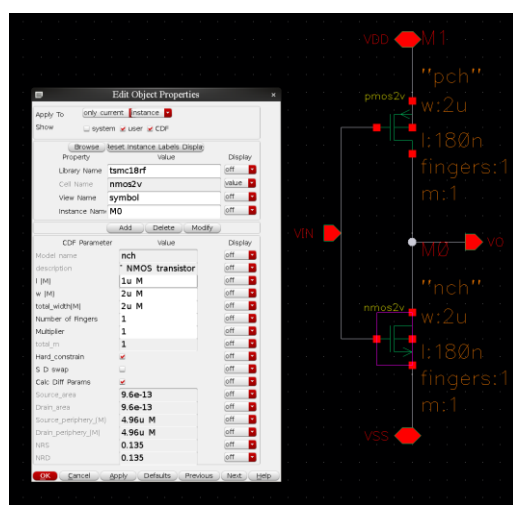- Change the L and W of the MOSFETs by selecting the instance and press “q”. Do this step for NMOS and PMOS using the following table.



	L (μm)	W (μm)
M0	1	2
M1	1	6

- Check and save

 

Outlines







- ☐ Objective
- ☐ CMOS Inverter
- ☐ Schematic Editor
- ☐ **Create Symbol**
- ☐ Testbench
- ☐ Cadence Hot Keys
- ☐ Discussion






Create Symbol

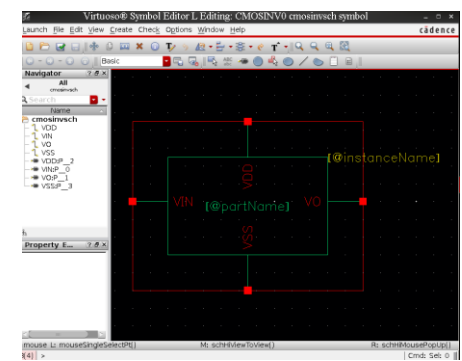 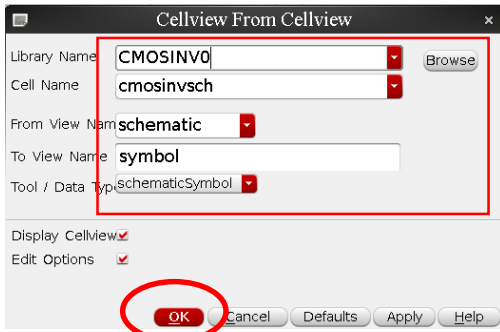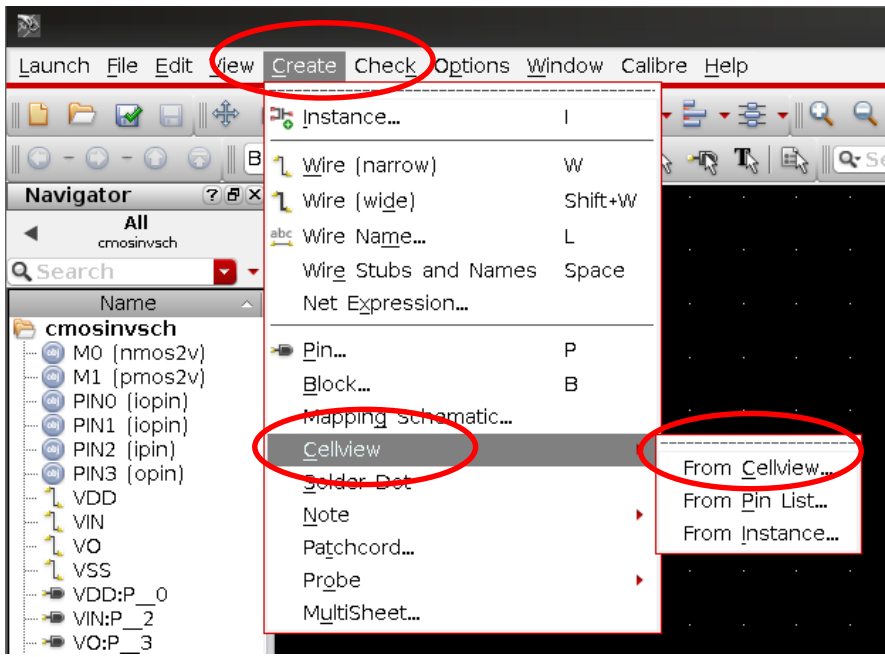❑ To create a symbol create → cellview → from cellview



Remove the red box and green box

 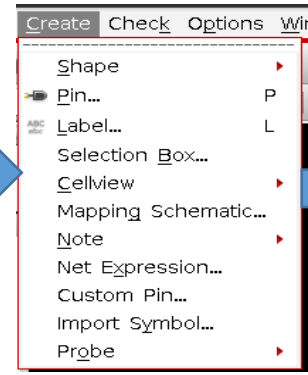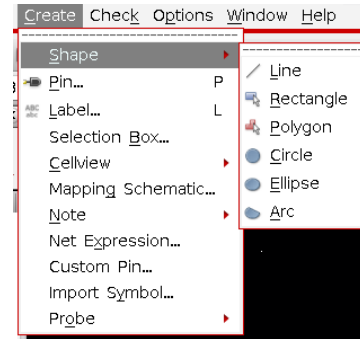❑ Shape of the symbol can be adjusted using create → line/circle



Outlines




- ☐ Objective
- ☐ CMOS Inverter
- ☐ Schematic Editor
- ☐ Create Symbol
- ☒ **Testbench**
- ☐ Cadence Hot Keys
- ☐ Discussion


Testbench (1/3)



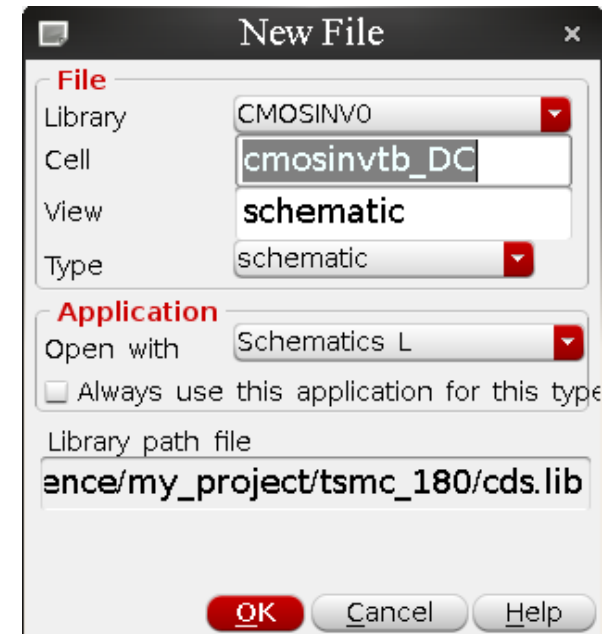
- ❑ Create a testbench for DC sweep
- File → new → cellview




- ❑ Add you symbol

 

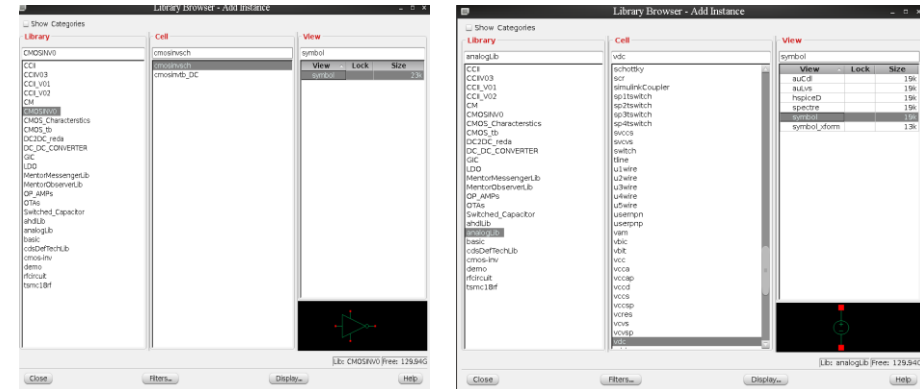- ❑ Select your symbol lib, cell, and cell view
- ❑ Add DC power supply, gnd, and Cap from analog lib



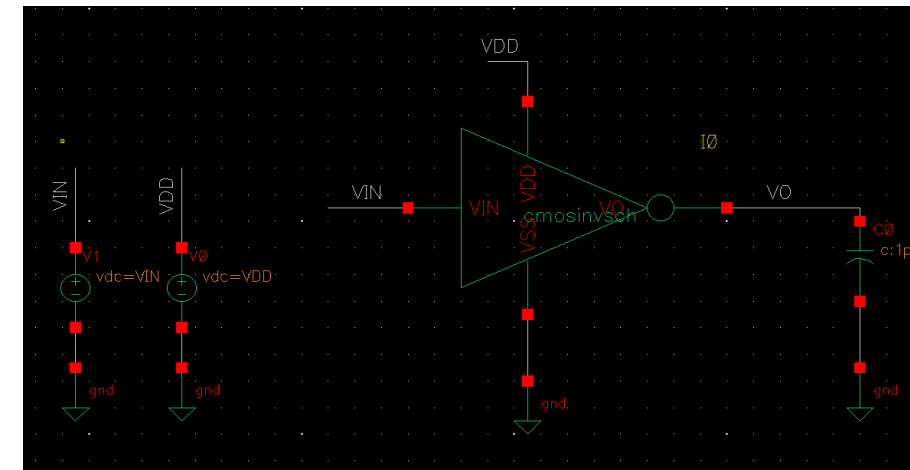
- ❑ Then, wire and add wire's labels using "I"





Testbench (2/3)



❑ To start the simulation

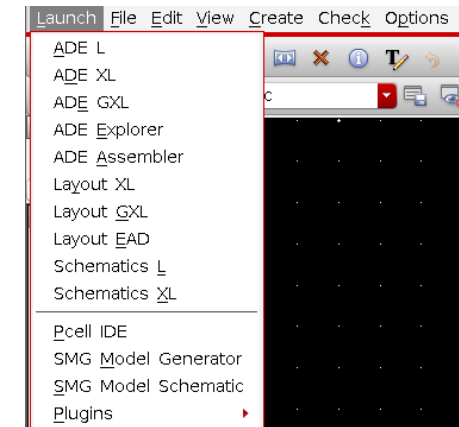


❑ Adjust the ADE as following and run

 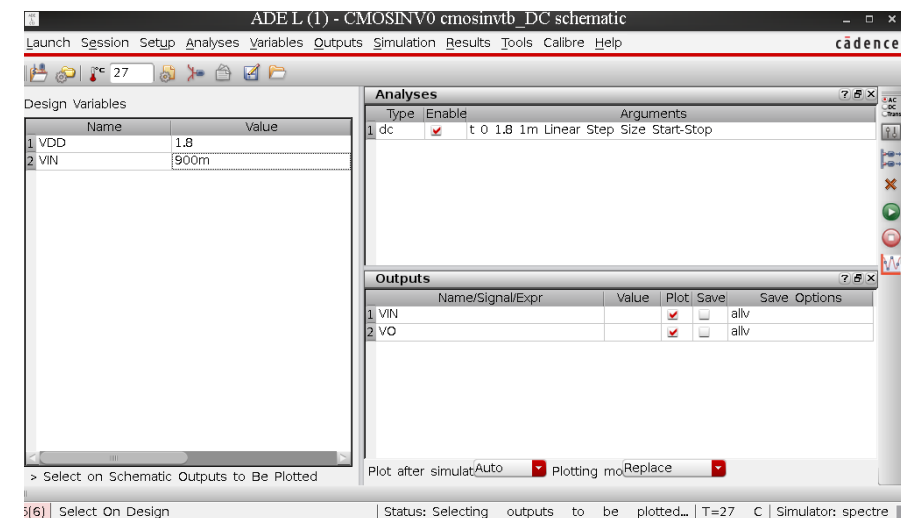



Testbench (3/3)



❑ To start the transient simulation

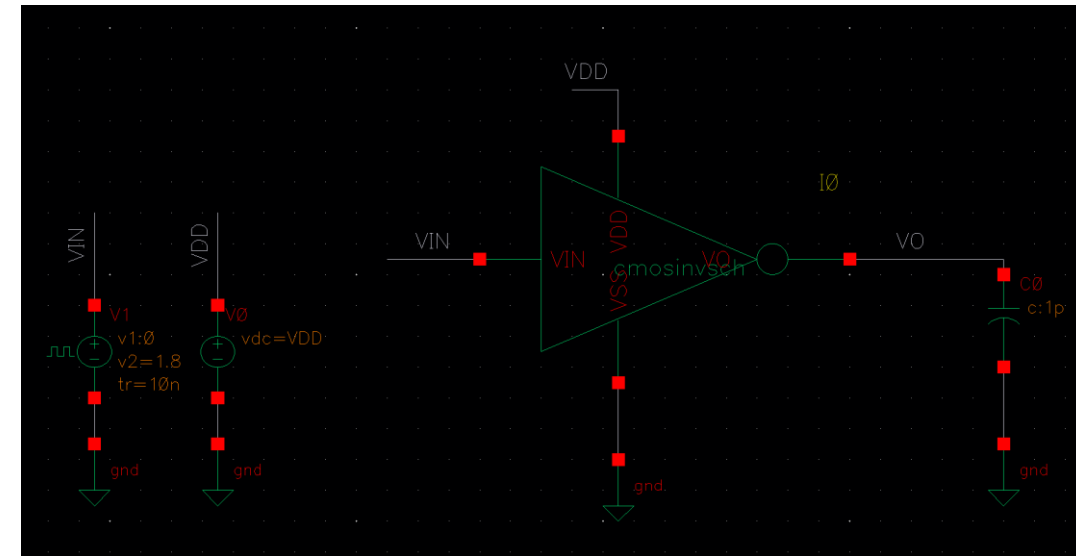

❑ Adjust the ADE as following and run

 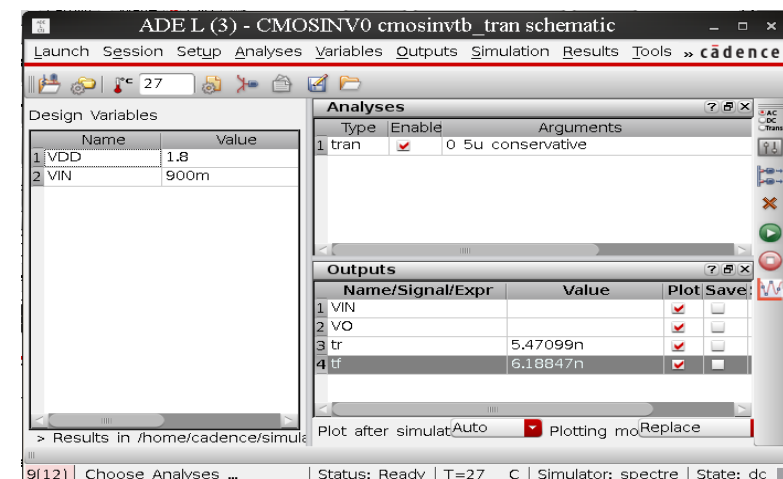

```
tr= cross(v("/VO" ?result "tran") 1.62 1 "rising" nil nil ) -  
cross(v("/VO" ?result "tran") 0.18 1 "rising" nil nil )
```

```
tf=(cross(v("/VO" ?result "tran") 0.18 1 "falling" nil nil) -  
cross(v("/VO" ?result "tran") 1.62 1 "falling" nil nil))
```

Outlines



- ☐ Objective
- ☐ CMOS Inverter
- ☐ Schematic Editor
- ☐ Create Symbol
- ☐ Testbench
- ☐ **Cadence Hot Keys**
- ☐ Discussion

Cadence Hot Keys



Frequently used for schematic editor

w	add a wire
i	add an instance
p	Add a pin
l	Label to a wire
e	display options like, grid size, snap size etc
q	select an object and press q to open the property dialogue box
shift-z	zoom-out by 2×
ctrl-z	zoom-in by 2×
c	copy
m	move: if you move an object, none of the wires connected to it move to maintain connectivity
S	stretch: if you stretch an object all connections to it also extend to maintain connectivity
u /shift-U	Undo/ redo
f	<i>fit</i> : fits the entire schematic in the window
shift-X	descend to edit by one
b /shift-b	to go one level up / to return to top

Outlines



- ☐ Objective
- ☐ CMOS Inverter
- ☐ Schematic Editor
- ☐ Create Symbol
- ☐ Testbench
- ☐ Cadence Hot Keys
- ☐ Discussion

Discussion



Thanks!